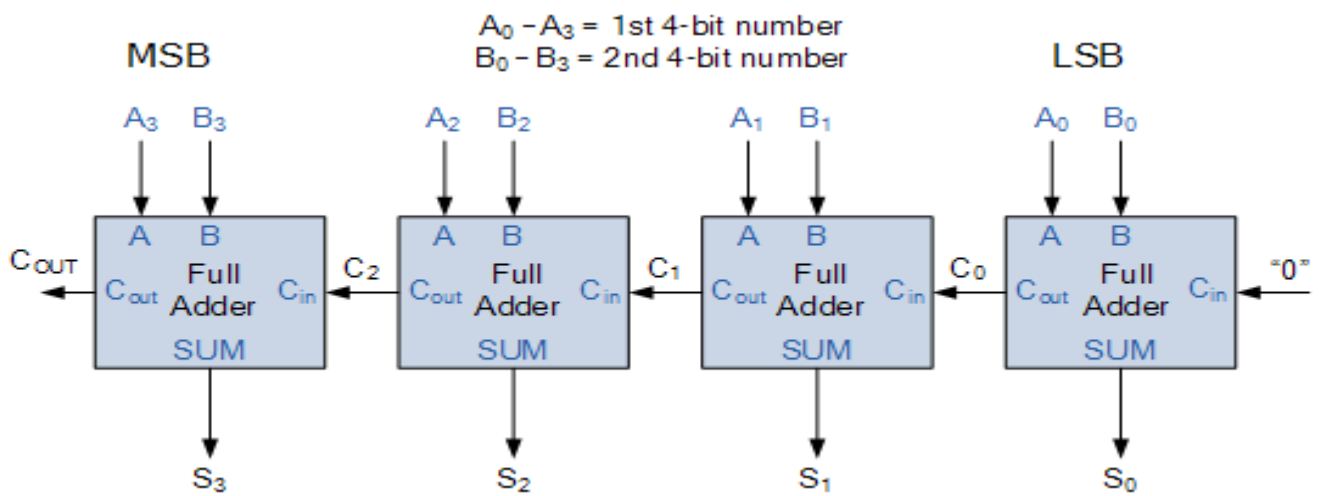


Title: Design and Implementation of Digital Circuits in Microwind

1. 4-Bit Full Adder

Circuit Diagrams:



Truth Tables: -

A	B	Cin	Sum	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Logic Equations: -


The sum (S) of the full-adder is the XOR of A, B, and Cin. Therefore,

$$\text{Sum, } S = A \oplus B \oplus C_{in} = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$


The carry (C) of the half-adder is the AND of A and B. Therefore,

$$\text{Carry, } C = AB + AC_{in} + BC_{in}$$


Microwind Layout: -

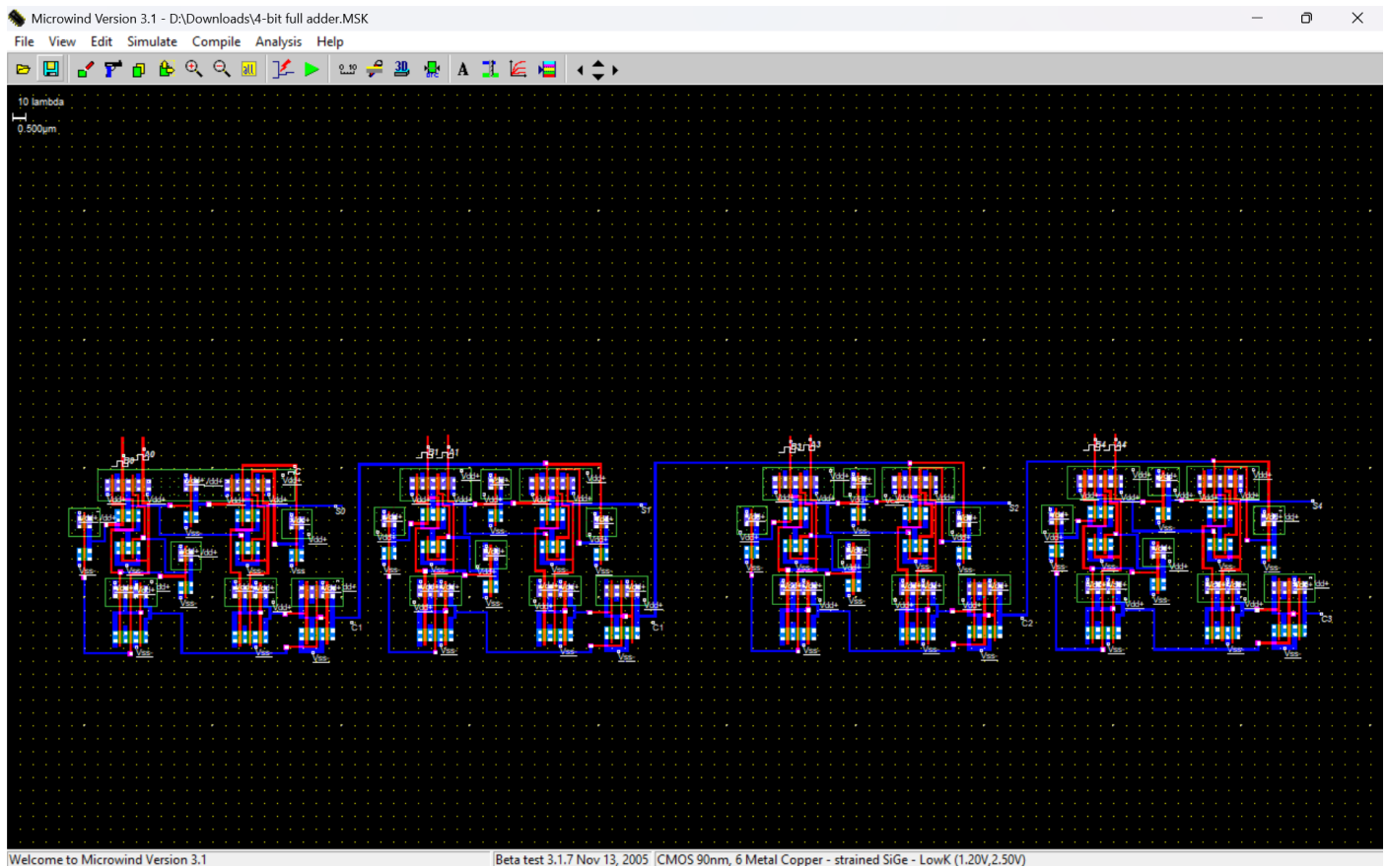

Output:

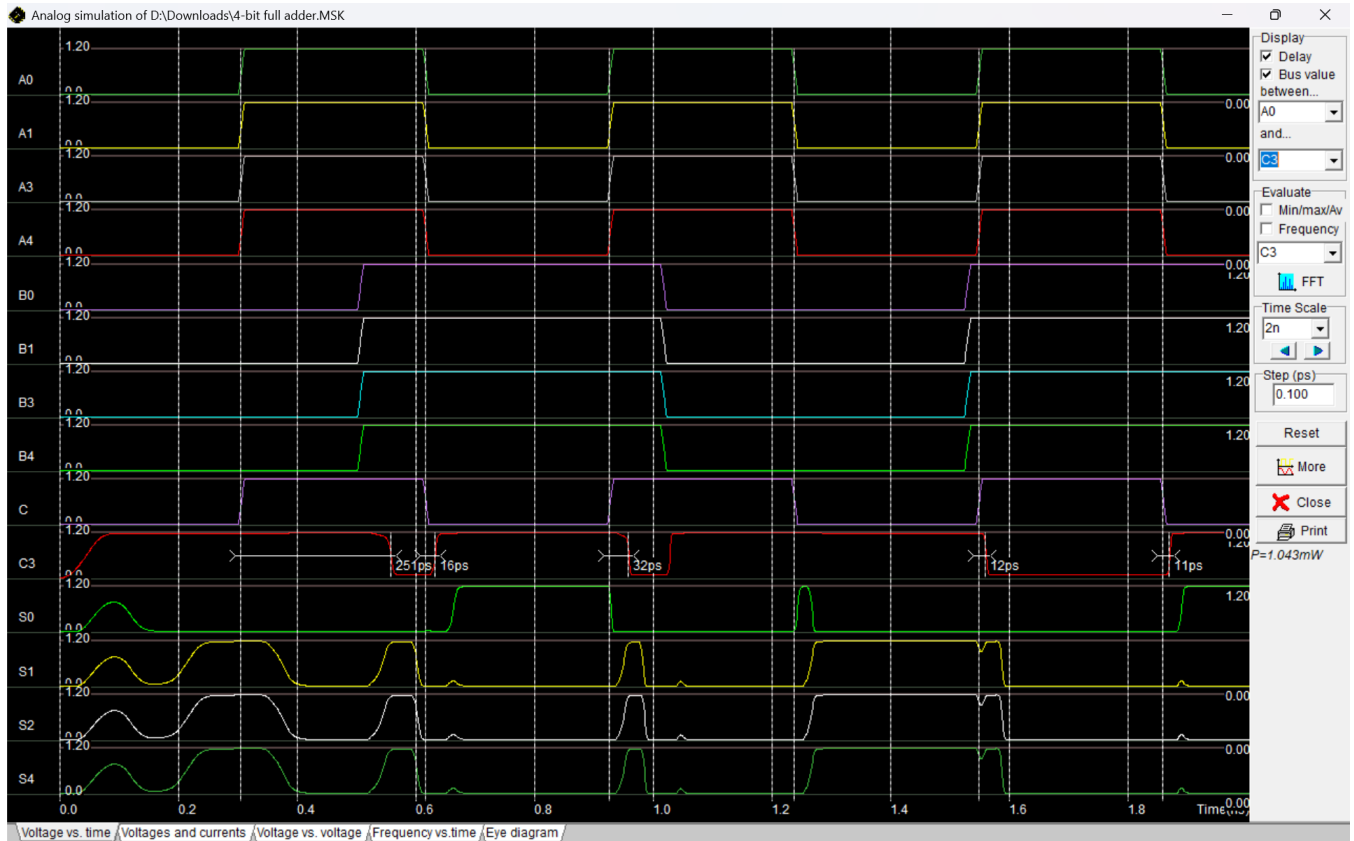

2. 8×1 Multiplexer Circuit Diagrams: -

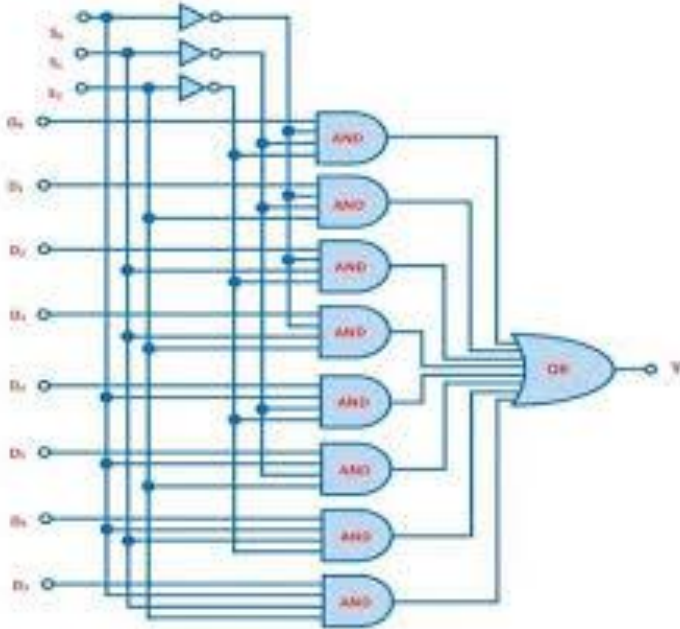

Block Diagram: -

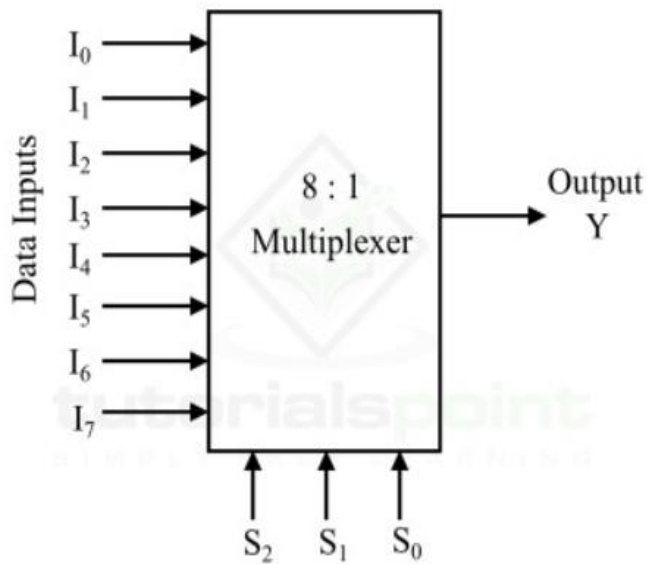



Figure 4 - 8:1 Multiplexer

Selection Inputs			Output
S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


Logic Equations: -

$$Y = S_2S_1S_0I_0 + S_2S_1S_0I_1 + S_2S_1S_0I_2 + S_2S_1S_0I_3 + S_2S_1S_0I_4 + S_2S_1S_0I_5 + S_2S_1S_0I_6 + S_2S_1S_0I_7$$

Microwind Layouts: -

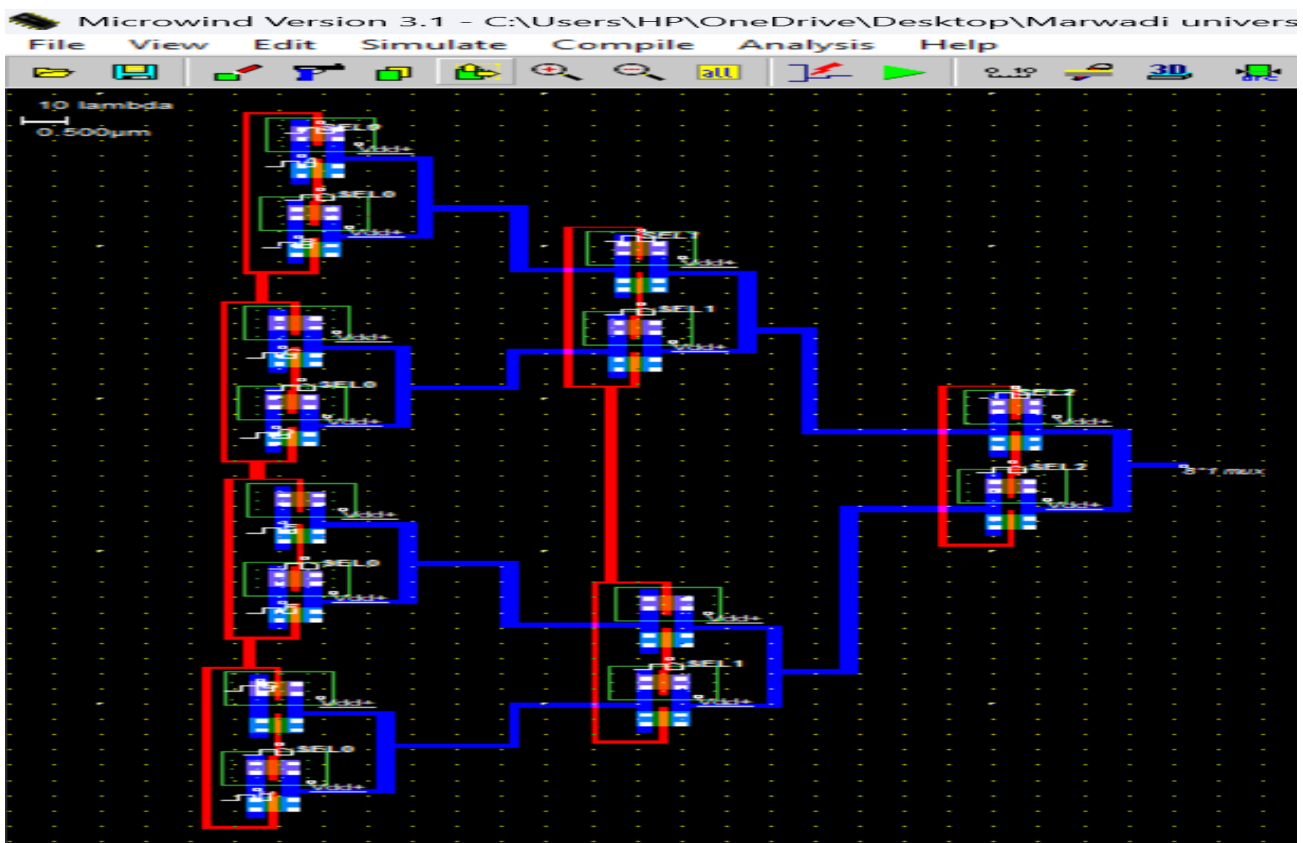


Output:

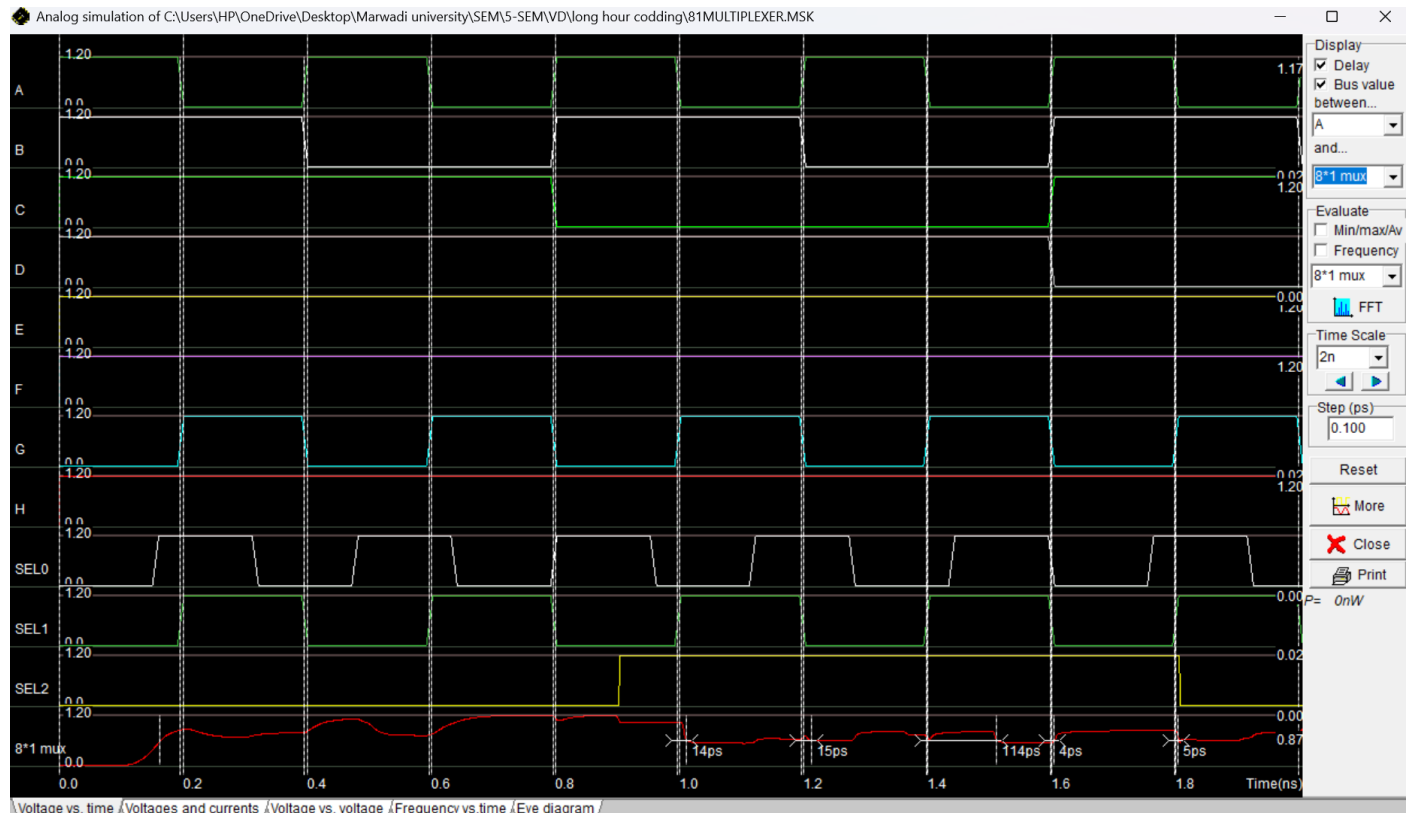

3. 1-bit Magnitude Comparator

Circuit Diagrams:

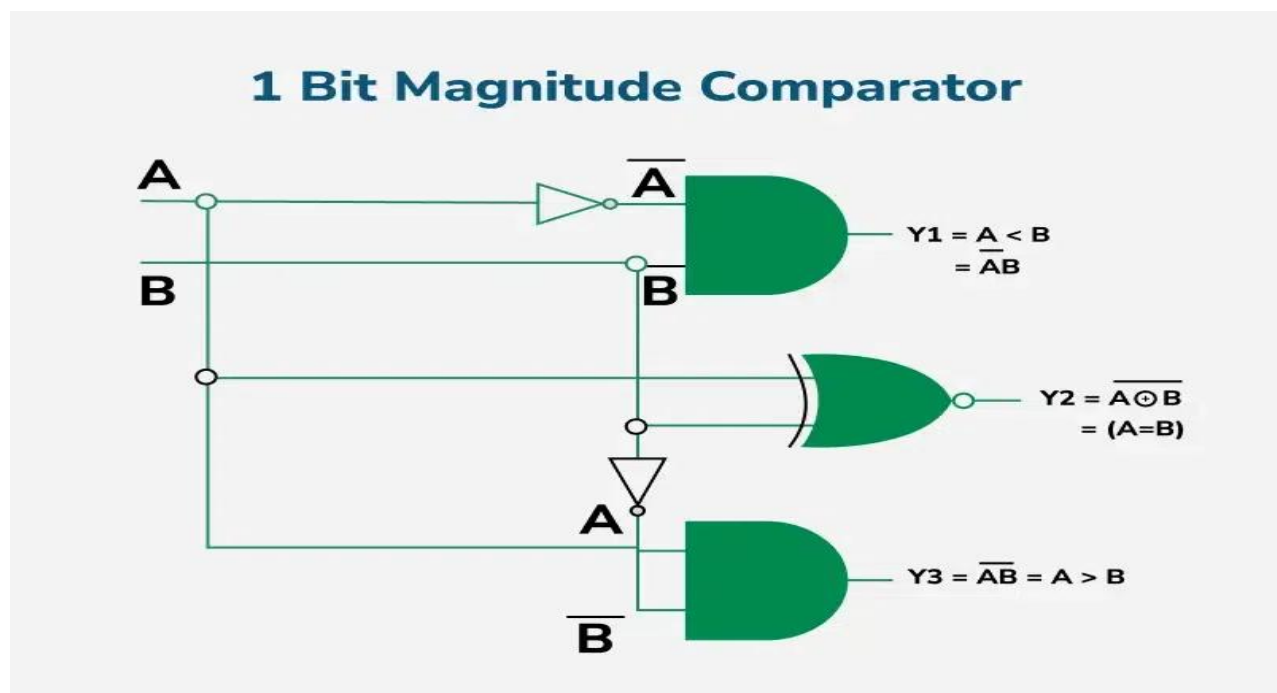

Truth Tables: -

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Logic Equations: -

$$(A < B) + (A > B) = A'B + AB'$$

Taking complement both sides

$$(A < B) + (A > B)' = (A'B + AB')'$$

$$(A < B) + (A > B)' = (A'B)' (AB)'$$

$$(A < B) + (A > B)' = (A + B') (A' + B)$$


$$(A < B) + (A > B)' = (AA' + AB + A'B' + BB')$$

$$= (AB + A'B')$$


Thus,

$$(A < B) + (A > B)' = (A = B)$$

Microwind Layouts: -

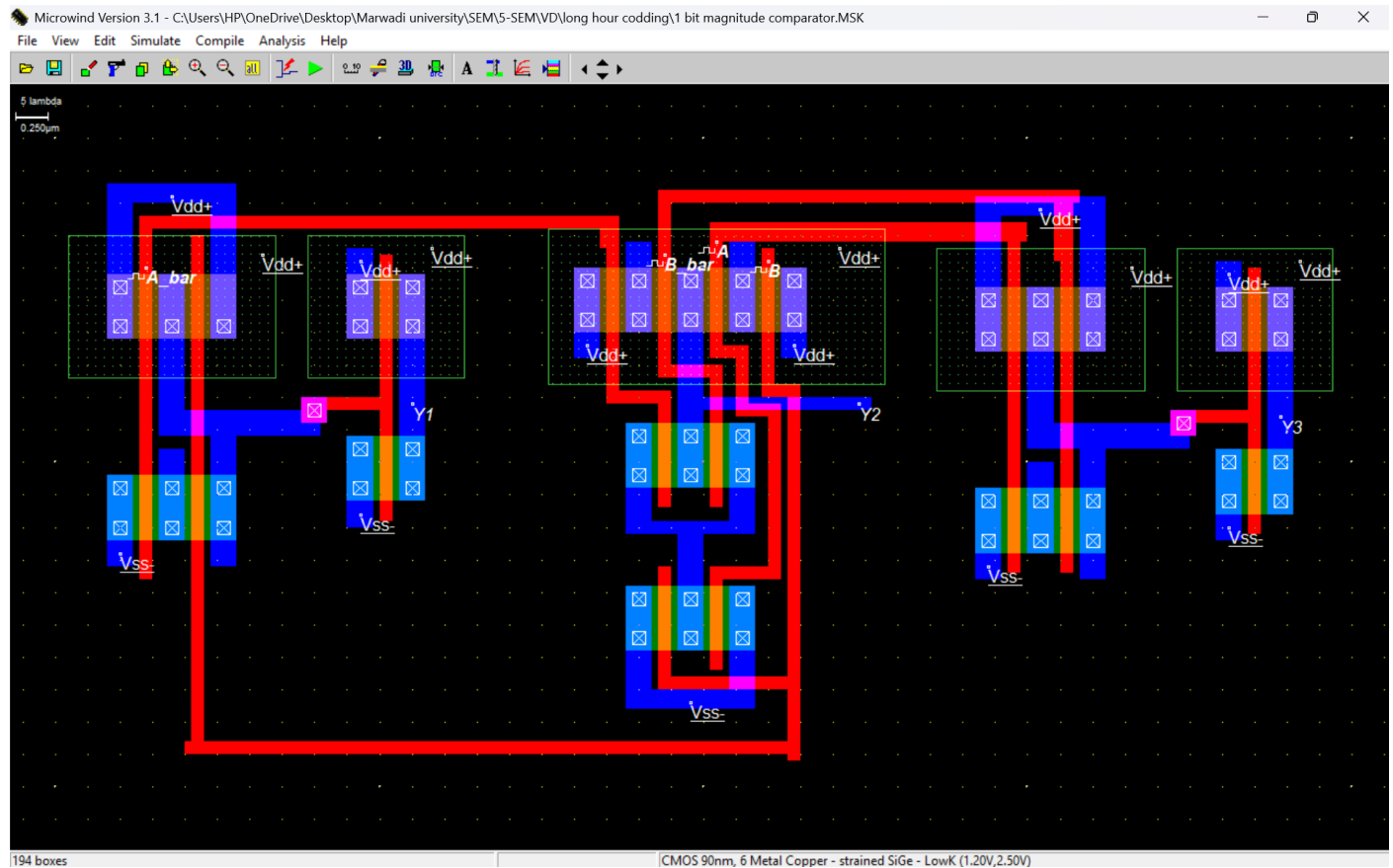


Output:

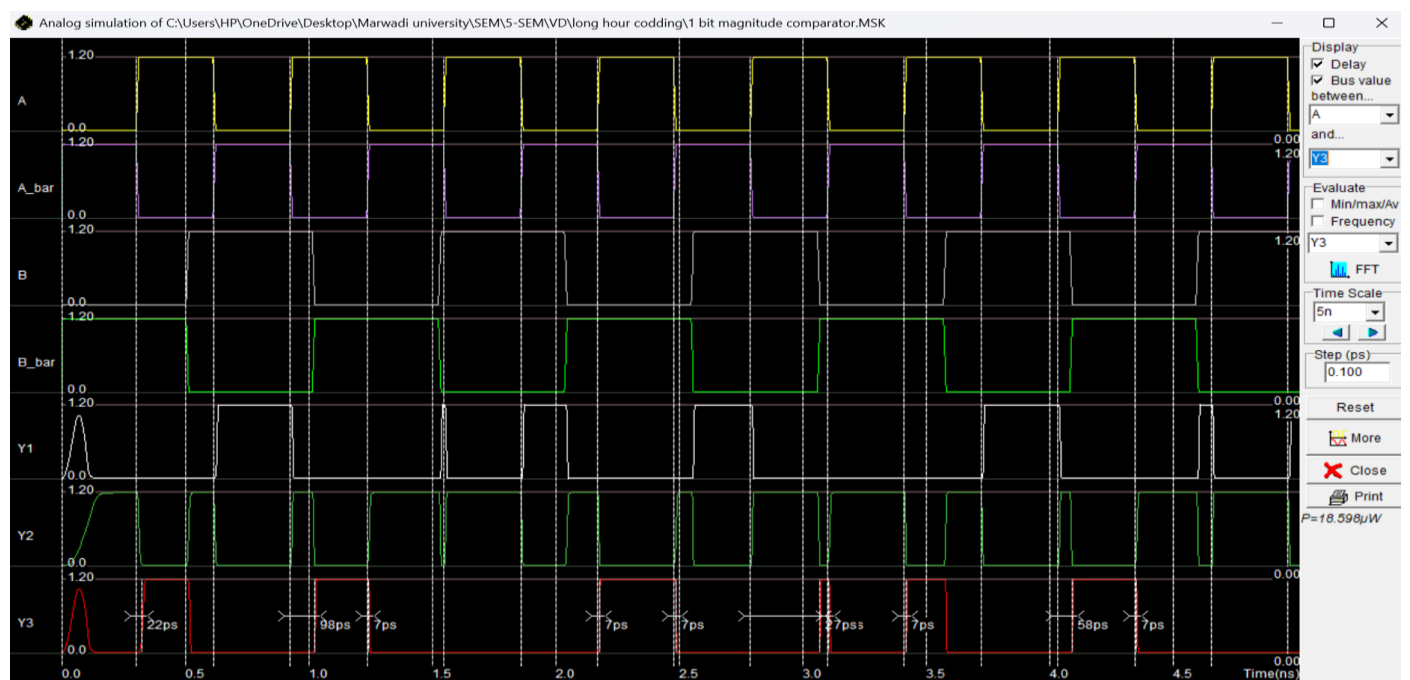

4. 4-bit Serial-In Serial-Out (SISO) Register


Circuit Diagrams: -

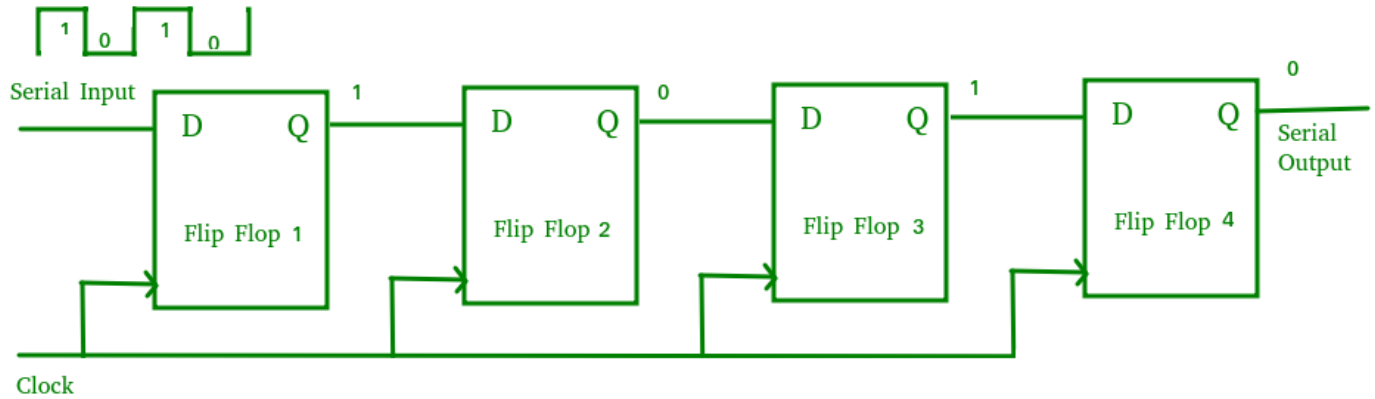


Truth table:

CLK	Q3	Q2	Q1	Q0
Initial (Reset)	0	0	0	0
After 1st clock pulse	1	0	0	0
After 2nd clock pulse	1	1	0	0
After 3rd clock pulse	1	1	1	0
After 4th clock pulse	1	1	1	1

Screenshots Of Layouts: -

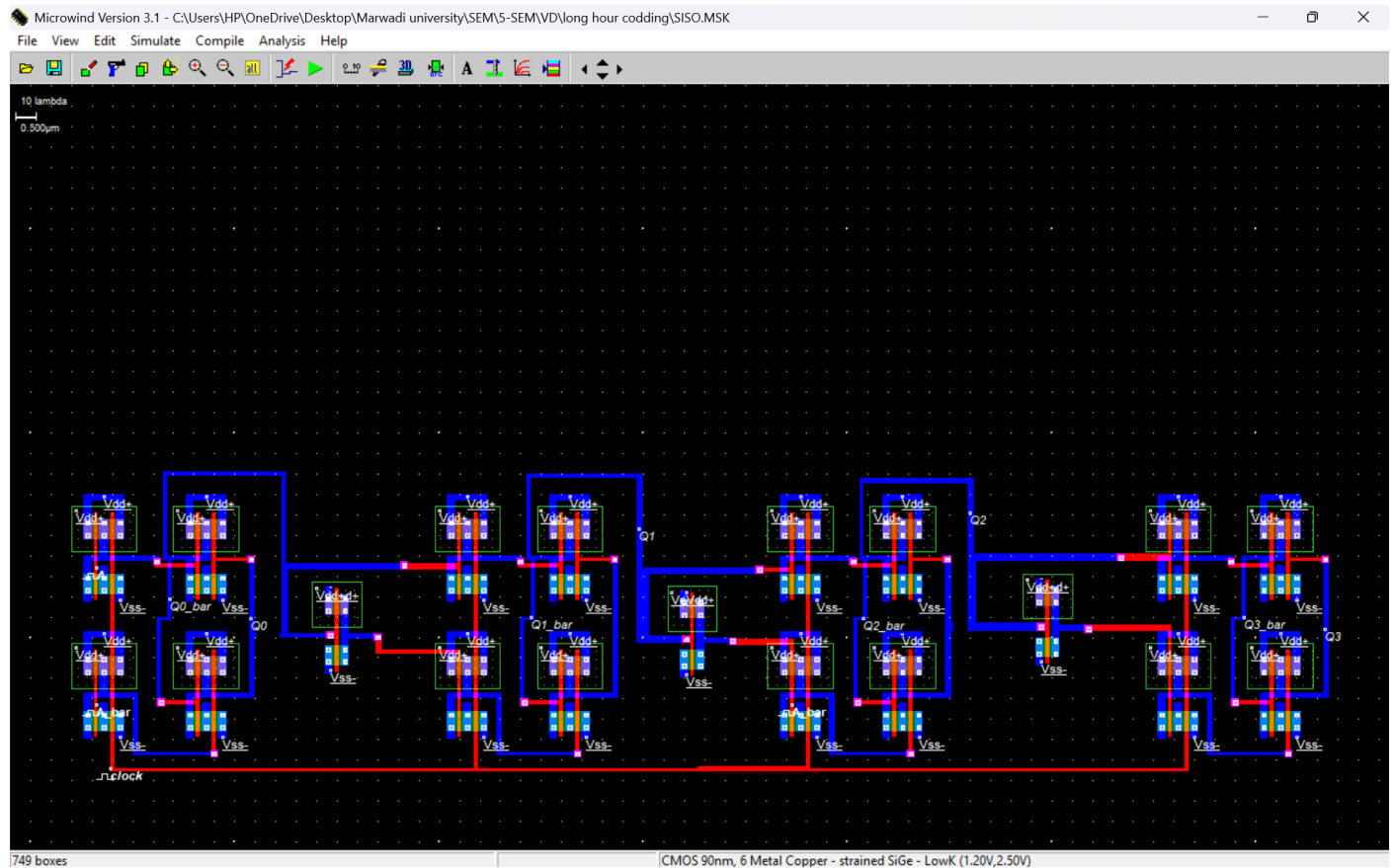

Output:

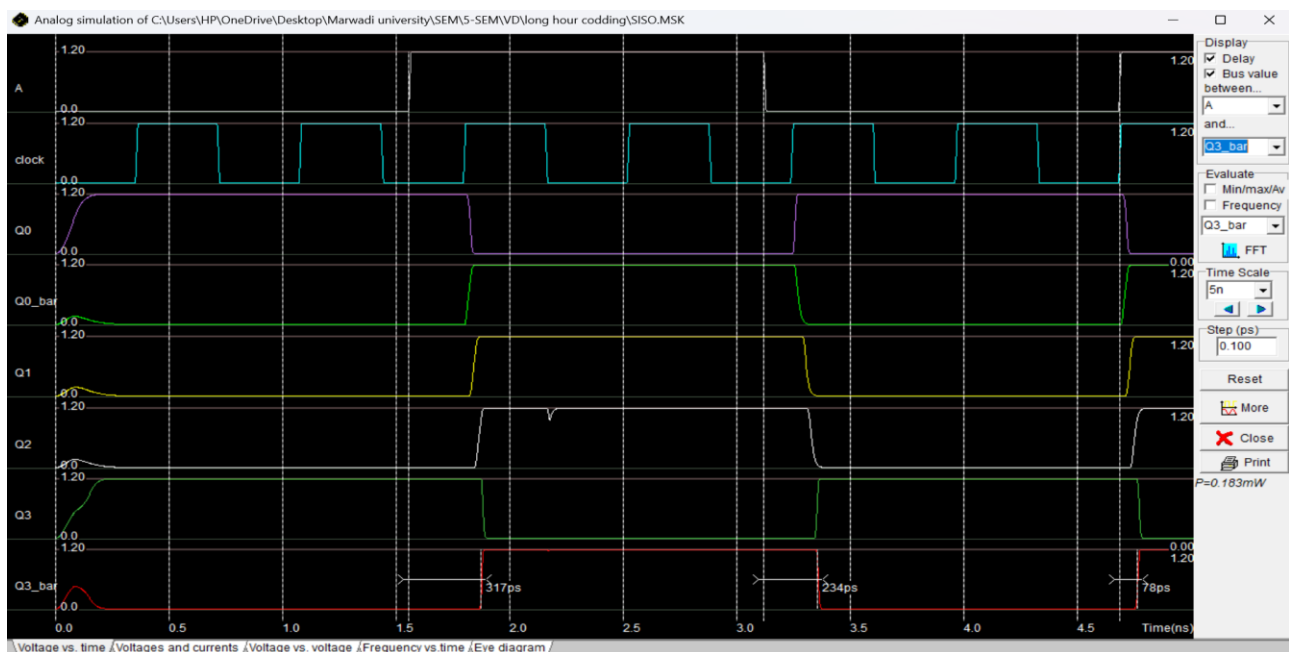

Department: - ICT
ENROLLMENT: - 92410133023

SUBJECT: - VLSI
DATE: - 13-09-2025

Conclusion:

Hence Design and implement the transistor level layout 4-bit Full Adder, 8×1 Multiplexer, 1-bit Magnitude Comparator and 4-bit Serial-In Serial-Out (SISO) Register using microwind.